

## Design Considerations for ISD1600B Series

AN-CC1001

---

### 1. Introduction

Winbond's ISD1600B Series is the first ChipCorder<sup>®</sup> product, which provides a Class D PWM speaker output with wide operating voltage, ranging from 2.4V to 5.5V. This PWM speaker driver maximizes audio volume and power efficiency. However, without adequate system power supply and distribution design, can result in higher noise levels than a typical speaker driver. Also, as usual, higher operating voltage induces more power noise on the system. As a result, it increases the challenges in optimizing the voice quality on an end-product.

This application note discusses the crucial factors for considerations while implementing ISD1600B Series. Then proposes some simple and cost-effective recommendations.

### 2. Decoupling Capacitors


In addition to the typical 0.1 $\mu$ F capacitor on the power lines, when a 10 $\mu$ F Aluminum Electrolytic capacitor is added to each  $V_{CCA}$ ,  $V_{CCD}$  and  $V_{CCP}$  power line, they can substantially reduce the noise from the power supplies. The locations of these capacitors should be as close to the device as possible. By doing so, it enhances the voice quality. Sometimes, a 4.7 $\mu$ F Aluminum Electrolytic capacitor may be sufficient for certain applications. Furthermore, we have experienced that the SMT capacitor reduces the noise, but the result may not be as good as that using the Aluminum Electrolytic type.

### 3. Layout Techniques


A good practice is to separate each power line ( $V_{CCA}$ ,  $V_{CCD}$  &  $V_{CCP}$ ) and each ground path ( $V_{SSA}$ ,  $V_{SSD}$  &  $V_{SSP}$ ) individually from the device to the system. Meanwhile, the ISD1600B device has designed with isolated  $V_{CCP}$  &  $V_{SSP}$  pads for PWM speaker driver. To minimize the noise from the PWM speaker driver, it is vital to route independent trace from each related pin to the system supply and ground terminals directly. The following items should be taken into accounts:

- Place  $V_{SSA}$  and  $V_{SSD}$  planes/paths on one side of PCB, then the  $V_{SSP}$  plane/path on the opposite side of PCB.
- Make each  $V_{SSA}$  and  $V_{SSD}$  as one big ground plane and as large as possible. Size the  $V_{SSA}$  and  $V_{SSD}$  planes in approximately equivalent area.
- Layout the  $V_{SSP}$  trace as large as possible and connect it to the system ground in the shortest distance.
- Funnel each ground path back to ground terminal for better grounding effect.
- Similarly, apply independent path technique on  $V_{CCA}$ ,  $V_{CCD}$  and  $V_{CCP}$  signals.
- The decoupling capacitors should be as close to the device as possible.
- Also, avoid running the signal traces close to the  $V_{CCP}$  and  $V_{SSP}$  traces.

## 3.1 Layout Example

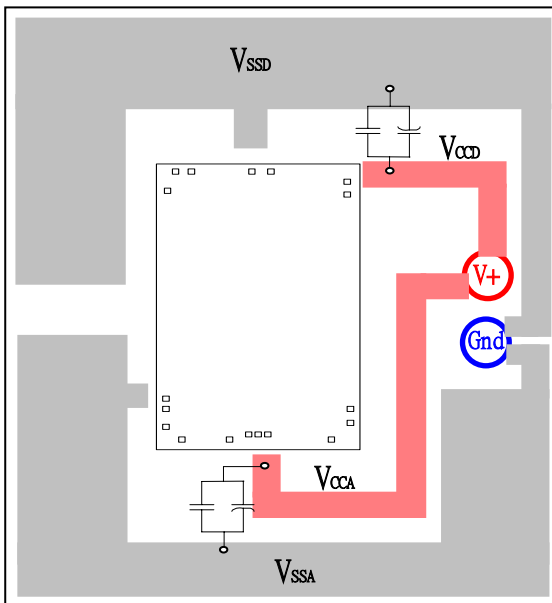

**Fig. 1: Top view of PCB**

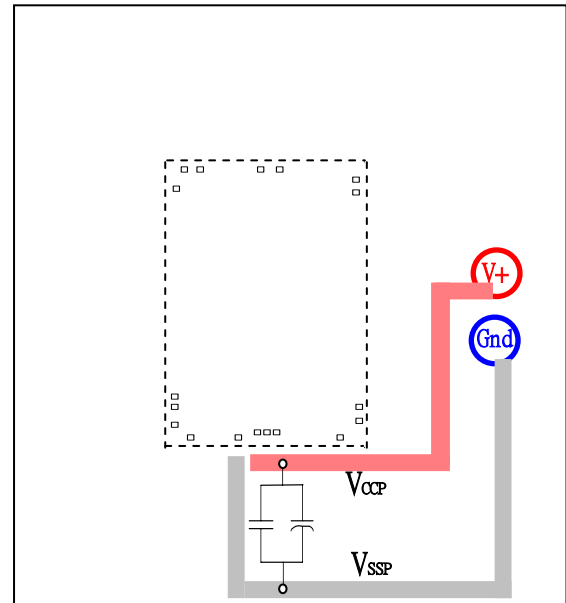

**Fig. 2: Bottom view of PCB**

The above example represents a generic layout for ISD1600B device. In the diagram, the die is magnified in order to show clearly the locations of the related power and ground pads, as well as the components. Hence, the illustrations are not in 1:1 ratio.

## 4. Dimension of PCB

### Experiment 1:


The first experiment uses a large PCB. The layout follows the above guidelines with both 0.1 $\mu$ F and 10 $\mu$ F capacitors installed on all  $V_{CCA}$ ,  $V_{CCD}$  and  $V_{CCP}$  power lines. It produces excellent voice quality on the recorded message.

If the 10 $\mu$ F capacitors are removed from the power lines, the voice quality slightly degrades. However, it may still be acceptable for some kinds of applications. The PCB dimension is approximately 3 inches x 2 ¼ inches. Fig. 3 shows the 1:1 ratio of the size of the PCB.


### Experiment 2:

In the second experiment which tries to simulate the practical case for mass production environment, a much smaller PCB is used. When both 0.1 $\mu$ F and 10 $\mu$ F capacitors are installed on all  $V_{CCA}$ ,  $V_{CCD}$  and  $V_{CCP}$  power lines, a very good voice quality is produced.

However, if the 10 $\mu$ F capacitors are changed to lower value or removed, the voice quality obviously degrades with distortions or noise, which may only be suitable for certain types of applications. Therefore, the existence of the Aluminum Electrolytic capacitor plays an important role to the quality required. In this case, the dimension of the PCB is about 1.1 inches x 1.5 inches, which is substantially smaller than that of Expt. 1. Fig. 4 shows the 1:1 ratio of the size of the PCB.

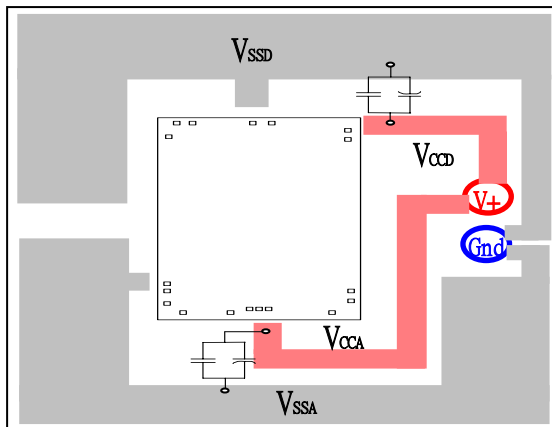

**Fig. 3: PCB Dimension of Expt. 1  
(1:1 ratio – PCB size)**

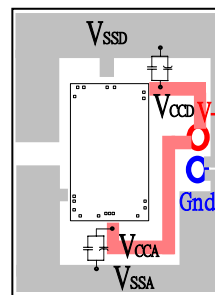

**Fig. 4: PCB Dimension of Expt. 2  
(1:1 ratio – PCB size)**

## 5. Recommendations

Generally, the quality of speaker engaged and the design of speaker housing are critical to the voice quality. The experimental results confirm that the voice quality can also be influenced by any or all of the following factors:

- The presence of the Aluminum Electrolytic decoupling capacitors on the power lines,
- Appropriate layout techniques,
- The dimension of the PCB.

Ideally implementing all above is strongly recommended. However, depending upon the specifications of the system and what level of voice quality are required for the applications, one can select an appropriate solution accordingly. Experiments are suggested in order to optimize for the best voice quality on the end-product. Nevertheless, there are trade-offs on which approach should be employed, pending upon the final products. Therefore, compromise may be necessary between the cost effectiveness and the voice quality.